

KOCAELİ UNIVERSITY ENGINEERING FACULTY

STEPPER MOTOR PMOD REFERENCE DOCUMENT

FURKAN YARDIMCI
2021-2022

DEPARTMENT: Electronic and Communication Engineering
TEACHER: Associate Professor ANIL ÇELEBİ

KOCAELİ, 2021

TABLE OF CONTENTS

TABLE OF CONTENTS	2
LIST OF FIGURES	2
LIST OF TABLES	2
PURPOSE OF THE PROJECT	3
INTRO/OVERVIEW	3
FEATURES	3
CONNECTIONS/INTERFACING	3
STEPPER MOTOR CONTROL	4
VERILOG HDL	5
•CODE	5-9
- PMOD_STEP_DRIVER.V	5-7
- CLOCK_DIV.V	8
- PMOD_STEP_INTERFACE.V	9
SCHEMATIC	10
BORD LAYOUT	10-12
MATERIAL LIST	13
REFERENCES	14

LIST OF FIGURES

STATE DIAGRAM OF THE CODE	5
SCHEMATIC OF THE CIRCUIT	10
TOP	10
BOTTOM	11
TOP/BOTTOM	11
FOTAGE OF THE CIRCUIT(TOP)	12
FOTAGE OF THE CIRCUIT(BOTTOM)	12
MATERIAL LIST	13

LIST OF TABLES

TABLE OF CONTENTS	4
PURPOSE OF THE PROJECT	4

PURPOSE:

The purpose of this document is to provide a document containing the necessary features about the design and use of stepper motor pmod, prepared by Kocaeli University Students FURKAN YARDIMCI and ASLINUR SERİN.

İNTRO/OVERWİEV:

The pmod stepper motor module provides the required number of headers to drive the 4-pin bipolar and 6-pin unipolar stepper motors with the Basys-3 board. Stepper motors are structures that contain magnets and coils that polarize this magnet to provide movement. When electric current passes through the coils in stepper motors, the motor creates torque due to the magnetic field created by this current. Each movement of this motor is called a step. The inputs of the Basys-3 card cannot provide this current required for the step motor to work. With the current/power amplifier circuit consisting of LM293D and mosfets on the pmod stepper module, it increases the low current it receives from the Basys-3 card to the levels that required for driving the stepper motor. In this way, the stepper motor is driven.

FEATURES:

- Stepper motor driver for 4 and 6-pin motors
- Can drive both motors simultaneously
- Multiple LEDs to indicate signal propagation
- Jumper for optional external power
- 2×6-pin pmod connector with GPIO interface

CONNECTIONS/INTERFACING:

The Pmod STEP communicates with the host board via the GPIO (General-purpose input/output) protocol. Microcontrollers usually include GPIOs. Depending on the application, a microcontroller's GPIOs may comprise its primary interface to external circuitry or they may be just one type of I/O used among several, such as analog signal I/O, counter/timer, and serial communication.

This Pmod offers headers for both 4-pin and 6-pin stepper motors. 4-pin stepper motors only work in the bipolar configuration, requiring that the two inputs on each electromagnetic coil are brought to the correct logic level voltages to induce current flow in the correct direction. The 6-pin stepper motor header on this Pmod can be oriented for either bipolar or unipolar configuration. The two extra pins on this header provide two positive power pins as a source of current for when an input on one end of a coil is driven to a logic low voltage level.

SM PMOD Reference Designator	Function
P2	This pin 2x6, right-angle header provides VCC, GND and (8) digital I/O signals from the Basy3's microcontroller to the SM PMOD through any of the Pmod connector ports on the Basys-3.

P3	4-wire stepper motor interface connector.
P4	6-wire stepper motor interface connector.
P9	This header provides access to pins 1-4 of the SM PMOD header J1 (labeled SIG1-SIG4 on the SM PMOD schematic).
P10	This header provides access to pins 5-8 of the SM PMOD header J1 (labeled SIG5-SIG8 on the SM PMOD schematic).
P7	GND
P8	GND
P6	External power screw terminal block. Provide power to the SM PMOD from an external source rather than from the Basys-3 board. NOTE: Pins 1 and 3 of P5 must be shorted (pins 2 and 3 of P5 open) to power the SM PMOD from an external source.
J1	External power measurement point. Use P7 or P8 (GND) on SM PMOD as the return to measure the voltage of the external power applied to the board.
P5	Power selection jumper. Jumper (short) pins 1 and 2 of P5 to supply power from the external power screw terminal block P6 or jumper (short) pins 2 and 3 of P5 to supply power from the Basys-3 board.
P1	Digital I/O signal state indication LED power jumper. Install the jumper (short pins 1 and 2) on P1 to provide power to bias the digital I/O signal state indication LEDs. Remove the jumper to reduce power consumption of board for battery powered applications.

TABLE 1.

STEPPER MOTOR CONTROL:

Stepper Motor Drive Sequence Code							
Decimal Value	Binary Value				Coil		Current Direction
	A	B	C	D	AB	CD	
8	1	0	0	0	ON	OFF	A -> B
10	1	0	1	0	ON	ON	A -> B, C -> D
2	0	0	1	0	OFF	ON	C -> D
6	0	1	1	0	ON	ON	B -> A, C -> D
4	0	1	0	0	ON	OFF	B -> A
5	0	1	0	1	ON	ON	B -> A, D -> C
1	0	0	0	1	OFF	ON	D -> C
9	1	0	0	1	ON	ON	A -> B, D -> C
8	1	0	0	0	ON	OFF	A -> B
10	1	0	1	0	ON	ON	A -> B, C -> D
2	0	0	1	0	OFF	ON	C -> D
6	0	1	1	0	ON	ON	B -> A, C -> D
4	0	1	0	0	ON	OFF	B -> A
5	0	1	0	1	ON	ON	B -> A, D -> C
1	0	0	0	1	OFF	ON	D -> C
9	1	0	0	1	ON	ON	A -> B, D -> C

TABLE 2

VERILOG HDL:

We used a state machine to evaluate multiple situations, as it can give various outputs according to the polarization status of the stepper motor coils. The state diagram is as follows.

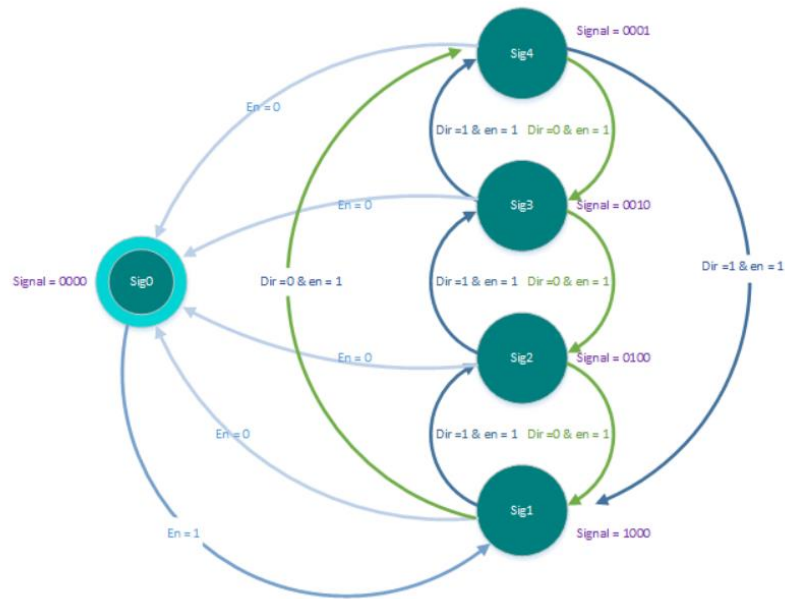


Image 1

CODE:

PMOD_STEP_DRIVER.V:

```

1  `timescale 1ns / 1ps
2
3  module pmod_step_driver(
4      input rst,
5      input dir,
6      input clk,
7      input en,
8      output reg [3:0] signal
9  );
10
11     // local parameters that hold the values of
12     // each of the states. This way the states
13     // can be referenced by name.
14     localparam sig4 = 3'b001;
15     localparam sig3 = 3'b011;
16     localparam sig2 = 3'b010;
17     localparam sig1 = 3'b110;
18     localparam sig0 = 3'b000;
19
20     // register values to hold the values
21     // of the present and next states.
22     reg [2:0] present_state, next_state;
23
24     // run when the present state, direction
25     // or enable signals change.
26     always @ (present_state, dir, en)
27     begin
28         // Based on the present state
29         // do something.
30         case(present_state)
31             // If the state is sig4, the state where
32             // the fourth signal is held high.

```

Stepper Motor PMOD Reference Document

```

33 : sig4:
34 : begin
35 :     // If direction is 0 and enable is high
36 :     // the next state is sig3. If direction
37 :     // is high and enable is high
38 :     // next state is sig1. If enable is low
39 :     // next state is sig0.
40 :     if (dir == 1'b0 && en == 1'b1)
41 :         next_state = sig3;
42 :     else if (dir == 1'b1 && en == 1'b1)
43 :         next_state = sig1;
44 :     else
45 :         next_state = sig0;
46 : end
47 : sig3:
48 : begin
49 :     // If direction is 0 and enable is high
50 :     // the next state is sig2. If direction
51 :     // is high and enable is high
52 :     // next state is sig4. If enable is low
53 :     // next state is sig0.
54 :     if (dir == 1'b0 && en == 1'b1)
55 :         next_state = sig2;
56 :     else if (dir == 1'b1 && en == 1'b1)
57 :         next_state = sig4;
58 :     else
59 :         next_state = sig0;
60 : end
61 : sig2:
62 : begin
63 :     // If direction is 0 and enable is high
64 :     // the next state is sig1. If direction
65 :     // is high and enable is high
66 :     // next state is sig3. If enable is low
67 :     // next state is sig0.
68 :     if (dir == 1'b0 && en == 1'b1)
69 :         next_state = sig1;
70 :     else if (dir == 1'b1 && en == 1'b1)
71 :         next_state = sig3;
72 :     else
73 :         next_state = sig0;
74 : end
75 : sig1:
76 : begin
77 :     // If direction is 0 and enable is high
78 :     // the next state is sig4. If direction
79 :     // is high and enable is high
80 :     // next state is sig2. If enable is low
81 :     // next state is sig0.
82 :     if (dir == 1'b0 && en == 1'b1)
83 :         next_state = sig4;
84 :     else if (dir == 1'b1 && en == 1'b1)
85 :         next_state = sig2;
86 :     else
87 :         next_state = sig0;
88 : end
89 : sig0:
90 : begin
91 :     // If enable is high
92 :     // the next state is sig1.
93 :     // If enable is low

```

```

94      // next state is sig0.
95      if (en == 1'b1)
96          next_state = sig1;
97      else
98          next_state = sig0;
99      end
100     default:
101         next_state = sig0;
102     endcase
103 end
104
105 // State register that passes the next
106 // state value to the present state
107 // on the positive edge of clock
108 // or reset.
109 always @ (posedge clk, posedge rst)
110 begin
111     if (rst == 1'b1)
112         present_state = sig0;
113     else
114         present_state = next_state;
115     end
116
117 // Output Logic
118 // Depending on the state
119 // output signal has a different
120 // value.
121 always @ (posedge clk)
122 begin
123     if (present_state == sig4)
124         signal = 4'b1000;
125     else if (present_state == sig3)
126         signal = 4'b0100;
127     else if (present_state == sig2)
128         signal = 4'b0010;
129     else if (present_state == sig1)
130         signal = 4'b0001;
131     else
132         signal = 4'b0000;
133     end
134 endmodule
135

```

CLOCK_DIV.V:

```

1  `timescale 1ns / 1ps
2
3  module clock_div(
4      input clk,
5      input rst,
6      output reg new_clk
7  );
8
9      // The constant that defines the clock speed.
10     // Since the system clock is 100MHZ,
11     // define_speed = 100MHZ/(2*desired_clock_frequency)
12     localparam define_speed = 26'd500000;
13
14     // Count value that counts to define_speed
15     reg [25:0] count;
16
17     // Run on the positive edge of the clk and rst signals
18
19     always @ (posedge(clk),posedge(rst))
20     begin
21         // When rst is high set count and new_clk to 0
22         if (rst == 1'b1)
23         begin
24             count = 26'b0;
25             new_clk = 1'b0;
26         end
27         // When the count has reached the constant
28         // reset count and toggle the output clock
29         else if (count == define_speed)
30         begin
31             count = 26'b0;
32             new_clk = ~new_clk;
33         end
34         // increment the clock and keep the output clock
35         // the same when the constant hasn't been reached
36         else
37         begin
38             count = count + 1'b1;
39             new_clk = new_clk;
40         end
41     end
42 endmodule

```


PMOD_STEP_INTERFACE.V:

```

1  `timescale 1ns / 1ps
2
3  module pmod_step_interface(
4      input clk,
5      input rst,
6      input direction,
7      input en,
8      output [3:0] signal_out
9  );
10
11      // Wire to connect the clock signal
12      // that controls the speed that the motor
13      // steps from the clock divider to the
14      // state machine.
15      wire new_clk_net;
16
17      // Clock Divider to take the on-board clock
18      // to the desired frequency.
19      clock_div clock_Div(
20          .clk(clk),
21          .rst(rst),
22          .new_clk(new_clk_net)
23      );
24
25      // The state machine that controls which
26      // signal on the stepper motor is high.
27      pmod_step_driver control(
28          .rst(rst),
29          .dir(direction),
30          .clk(new_clk_net),
31          .en(en),
32          .signal(signal_out)
33      );
34
35  endmodule
36

```

SCHEMATIC:

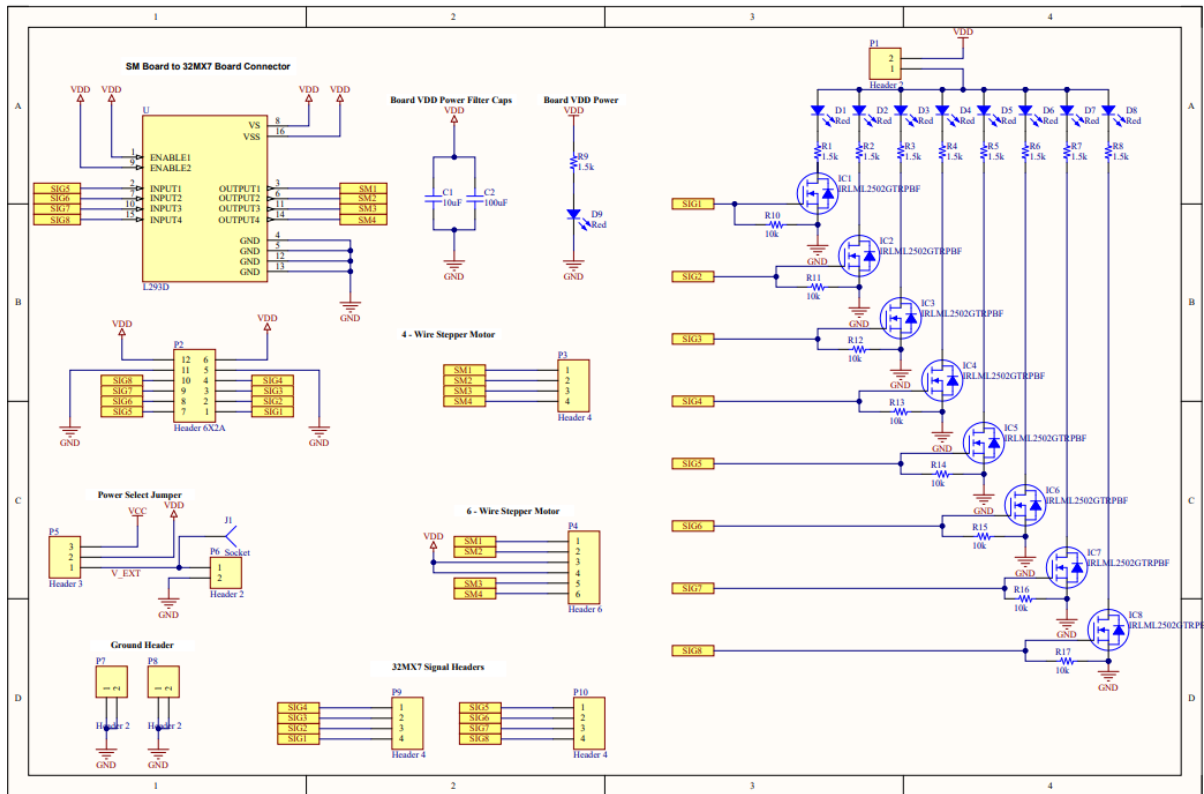


Image 2

BOARD LAYOUT:

TOP:

 


Image 3

BOTTOM:

 


Image 4

TOP/BOTTOM:

 


Image 5

 


Image 6

 


Image 7

MATERIALS LIST:

Comment	Description	Designator	Footprint	LibRef	Quantity
10uF	CAP CER 10UF 16V X5R 1206	C1	CAP 1206/3216	CL31A106KOCLNNC	1
100uF	CAP CER 100UF 6.3V X5R 1206	C2	CAP 1206/3216	CL31A107MQHNNNE	1
Red	LED RED CLEAR 1206 SMD	D1, D2, D3, D4, D5, D6, D7, D8, D9	LED 1206/3216 RED	SM1206NHC-IL	9
IRLML2502GTRPBF	MOSFET N-CH 20V 4.2A SOT-23-3	IC1, IC2, IC3, IC4, IC5, IC6, IC7, IC8	INFINEON SOT-23-3	IRLML2502GTRPBF	8
Socket	Socket	J1	PIN1	Socket	1
Header 2	Header, 2-Pin	P1, P6, P7, P8	HDR1X2	Header 2	4
Header 6X2A	Header, 6-Pin, Dual row	P2	HDR2X6_CEN	Header 6X2A	1
Header 4	Header, 4-Pin	P3, P9, P10	HDR1X4	Header 4	3
Header 6	Header, 6-Pin	P4	HDR1X6	Header 6	1
Header 3	Header, 3-Pin	P5	HDR1X3	Header 3	1
1.5k	RES SMD 1.5K OHM 1% 1/4W 1206	R1, R2, R3, R4, R5, R6, R7, R8, R9	RES 1206/3216	ERJ-8ENF1501V	9
10k	RES SMD 10K OHM 1% 1/4W 1206	R10, R11, R12, R13, R14, R15, R16, R17	RES 1206/3216	ERJ-8ENF1002V	8
L293D	Bipolar Motor Driver Parallel 16-PowerDIP	U	DIP880W50P254L200 0H510Q16	L293D	1

Image 8

REFERENCES:

- <https://www.elektrovadi.com/urun/pmod-step-motor-surucu-pmod-stepper>
- <https://digilent.com/reference/pmod/pmodstep/reference-manual?redirect=1>
- <https://www.robocombo.com/blog/icerik/step-motor-nedir-ne-ise-yarar-nasil-calisir>
- <https://digilent.com/reference/learn/fundamentals/communication-protocols/gpio/start>
- <https://www.instructables.com/How-to-Control-a-Stepper-Motor-With-an-FPGA/>
- https://www.youtube.com/watch?v=ePSCZ_DtF7c
- <https://howtomechatronics.com/how-it-works/electrical-engineering/stepper-motor/>